
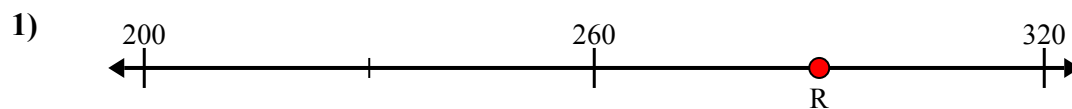


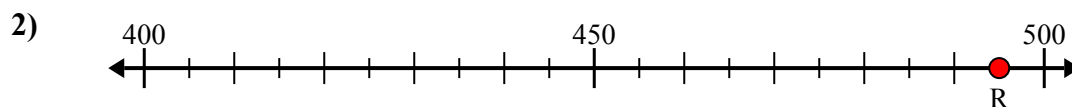


Найдите значение R.

Ответы


1. _____




2. _____

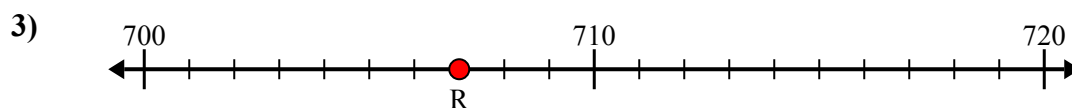


3. _____

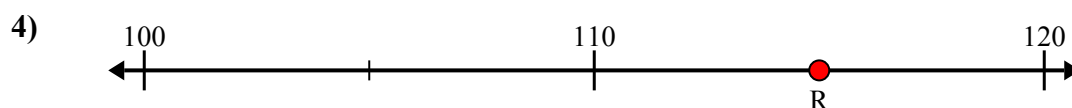


4. _____

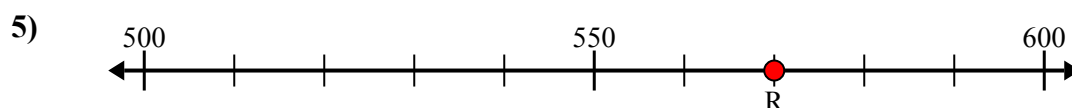


5. _____

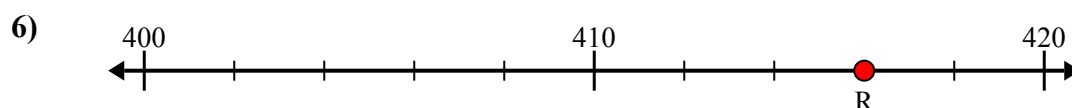


6. _____

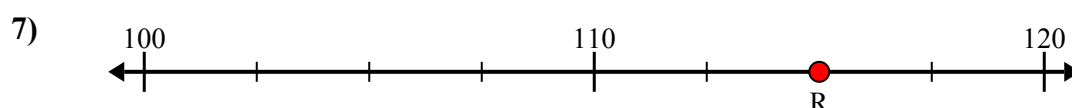


7. _____

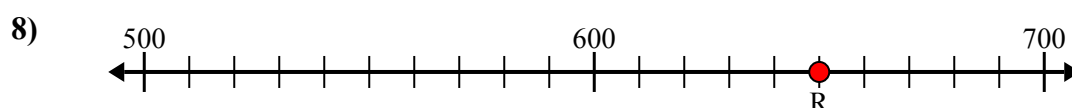

8. _____

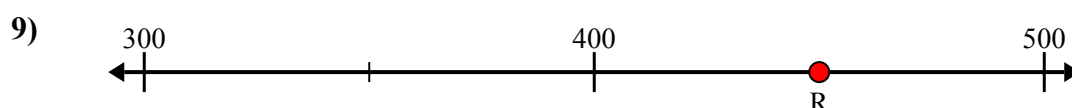











9. _____

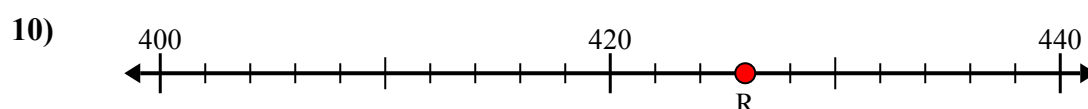

10. _____



Найдите значение R.

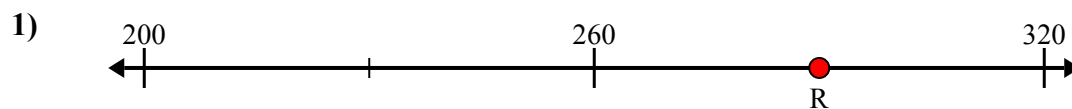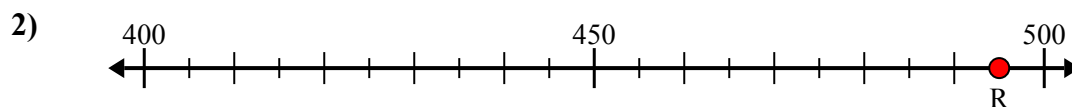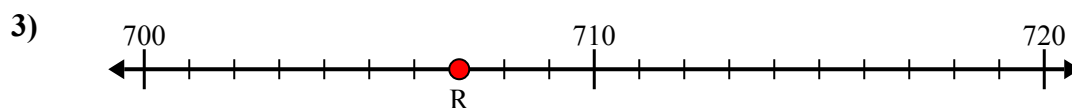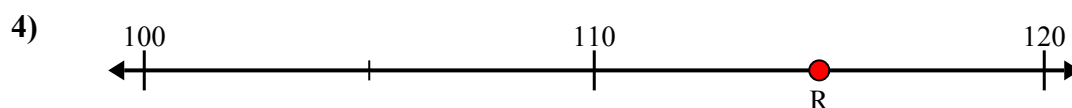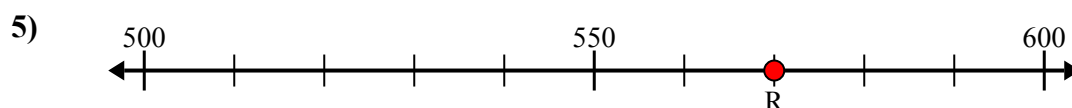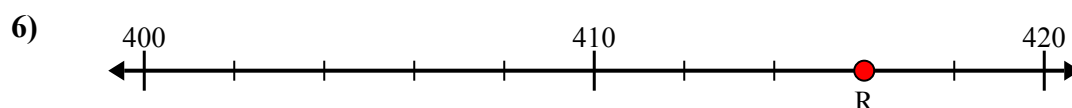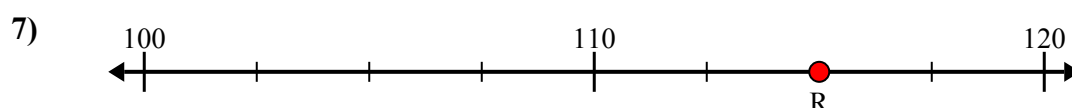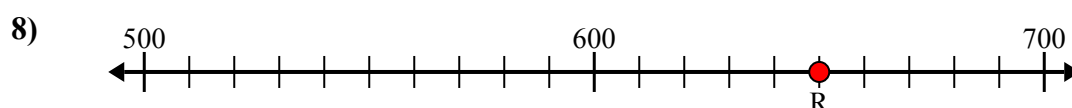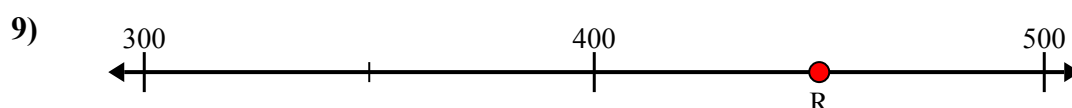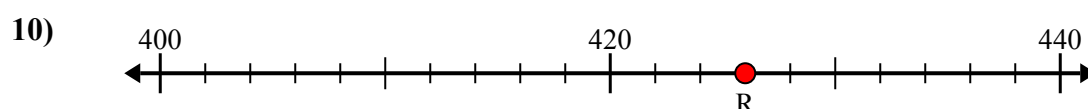Ответы1. 2902. 4953. 7074. 1155. 5706. 4167. 1158. 6509. 45010. 426